

Exam 3 Review


4/29/13

2012 Exam problem


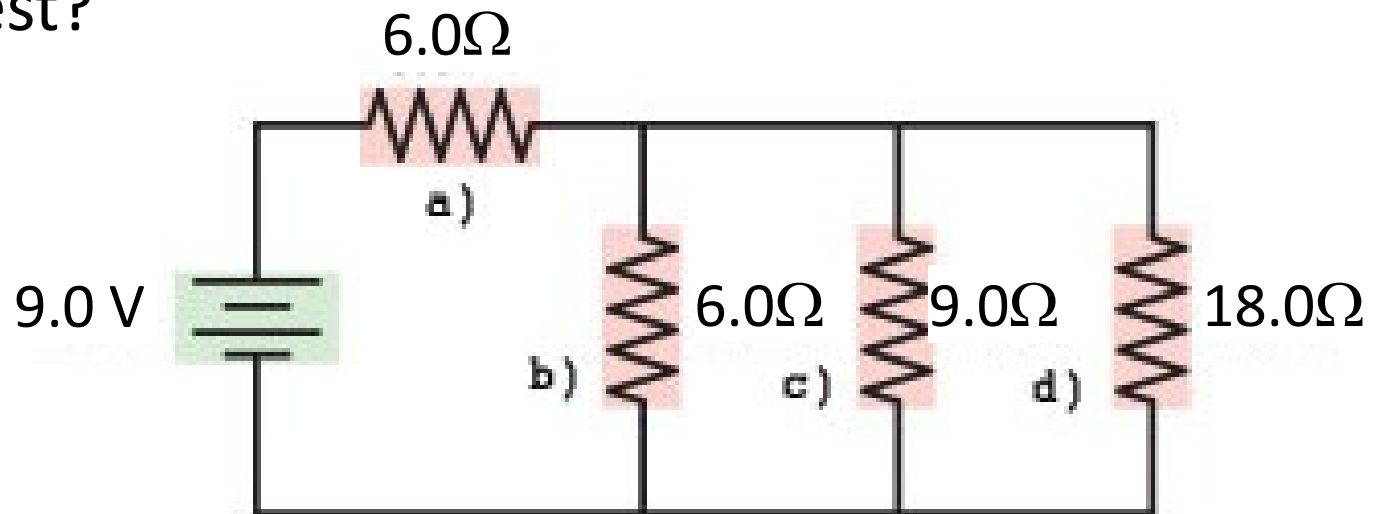
1. Two point charges are placed 12 meters apart. The charge on the left is $+10 \text{ nC}$ and the charge on the right is $+20 \text{ nC}$.
 - A. Find the electric field at a point between the charges, 4.0 meters from the $+20 \text{ nC}$ charge.
 - B. If an electron is placed between the charges, 4.0 meters from the $+20 \text{ nC}$ charge, find the electrostatic force on the electron.

Circuits

- For each resistor - a, b, c and d - find
 - Current through
 - Voltage across
 - Power dissipated
 - If these resistors are light bulbs, which is brightest?



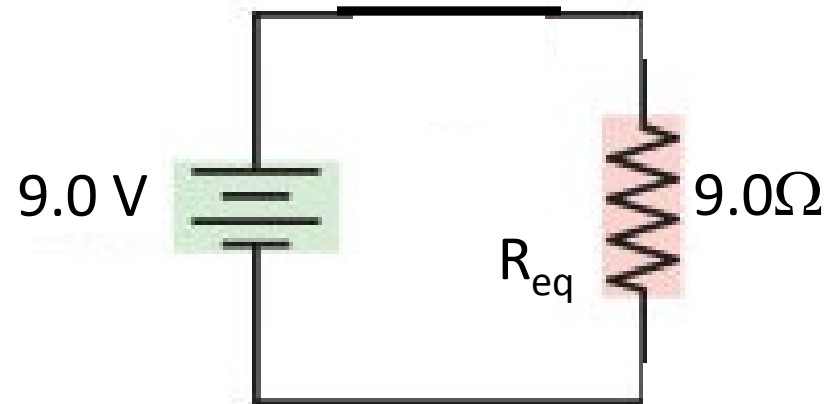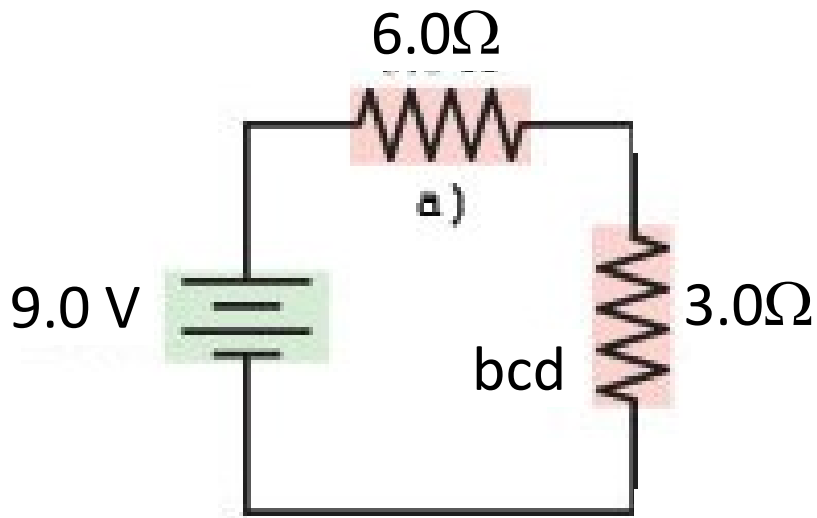- Step 1 – find the equivalent resistance of the circuit.




- Step 2 – Find total current through the circuit


$$V = IR$$

$$\text{So } I = V/R$$
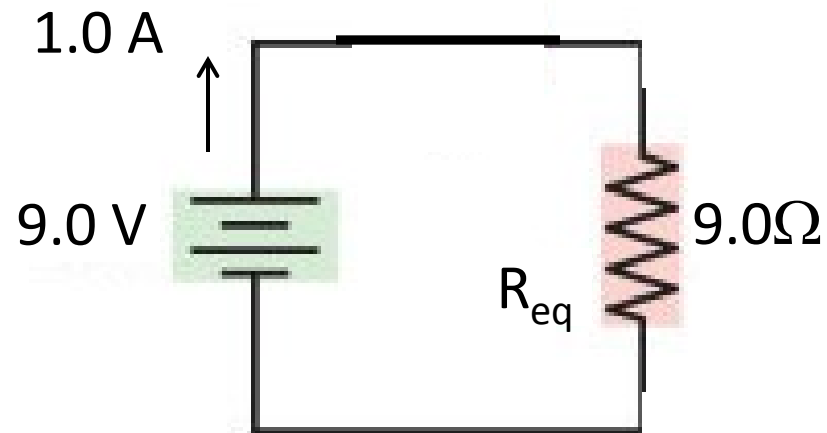
$$I = 9.0 \text{ V} / 9.0 \Omega = 1.0 \text{ A}$$



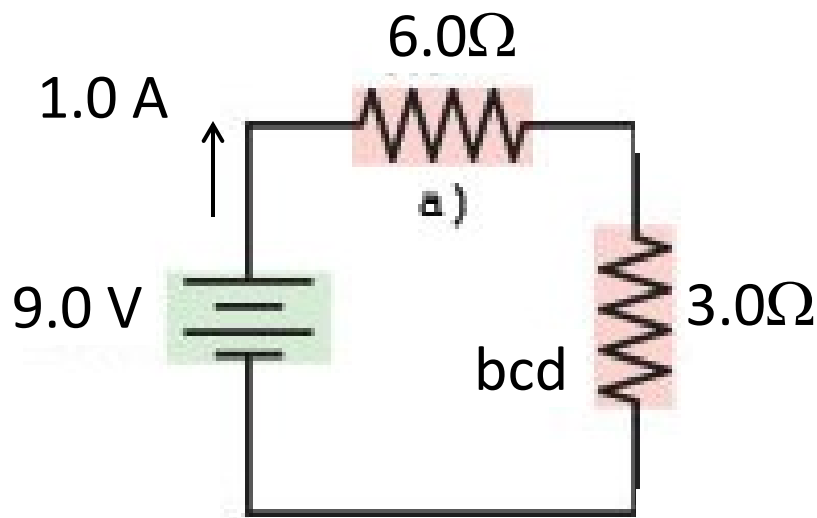- Step 3 – build back out one step at a time, finding voltage and current for each resistor as you build out.




$$V_a = 1.0\text{ A} * 6.0\Omega = 6.0\text{ V}$$

$$V_{bcd} = 1.0\text{ A} * 3.0\Omega = 3.0\text{ V}$$

$$\text{Check } 3.0\text{ V} + 6.0\text{ V} = 9.0\text{ V}$$

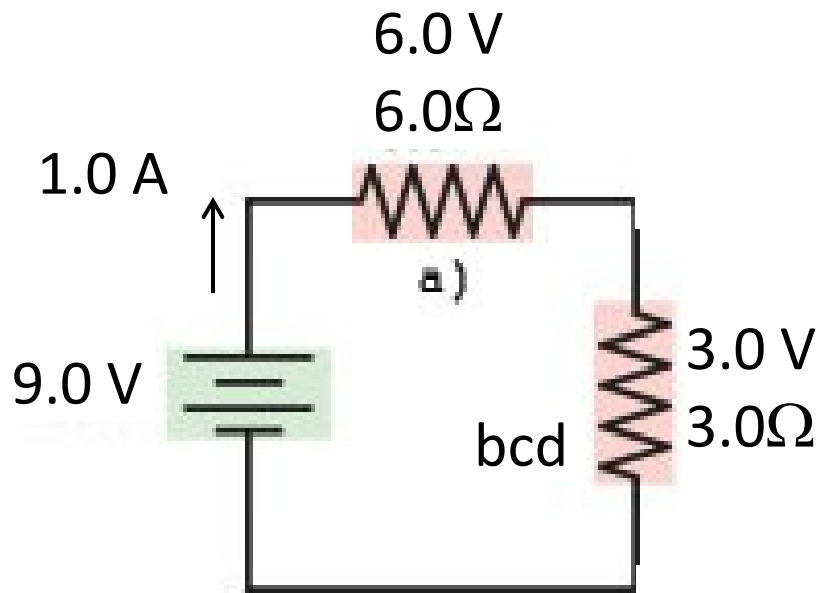- Step 3 – build back out one step at a time, finding voltage and current for each resistor as you build out.




$$V_a = 1.0\text{ A} * 6.0\Omega = 6.0\text{ V}$$

$$V_{bcd} = 1.0\text{ A} * 3.0\Omega = 3.0\text{ V}$$

$$\text{Check } 3.0\text{ V} + 6.0\text{ V} = 9.0\text{ V}$$

Label the circuit!

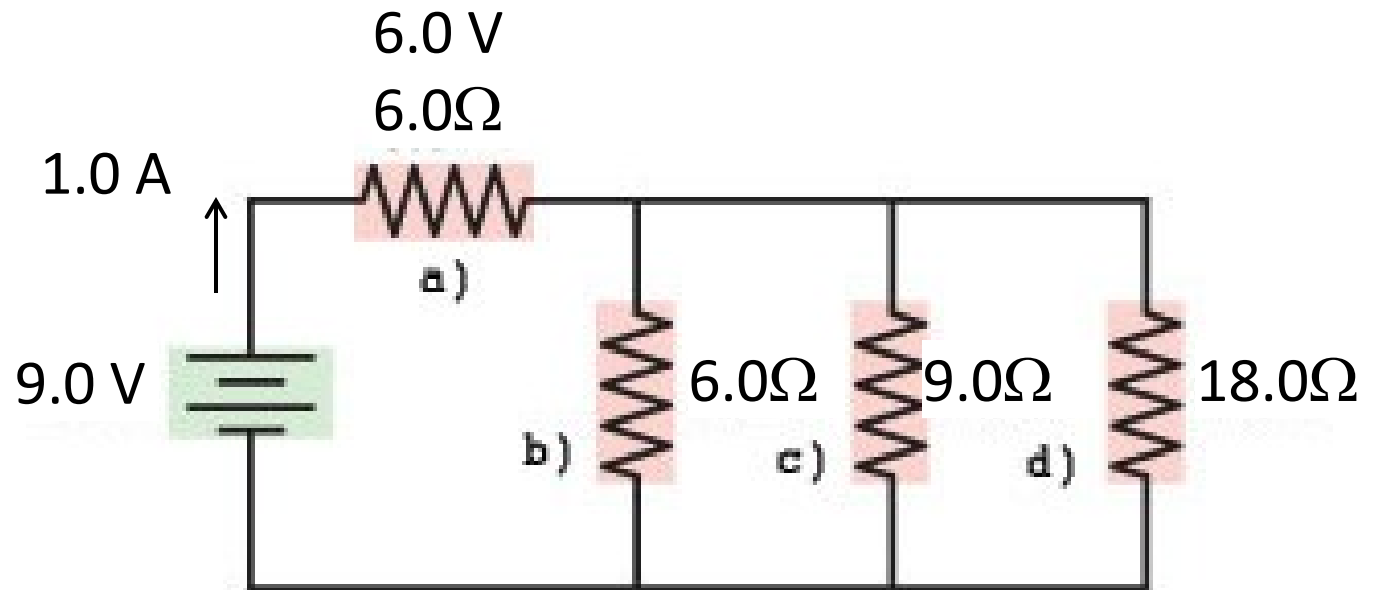- Now what do we know?
- Voltage or Current for b, c and/or d?




$$P_a = 6 \text{ W}$$

$$P_b = 1.5 \text{ W}$$

$$P_c = 1.0 \text{ W}$$

$$P_d = 0.5 \text{ W}$$

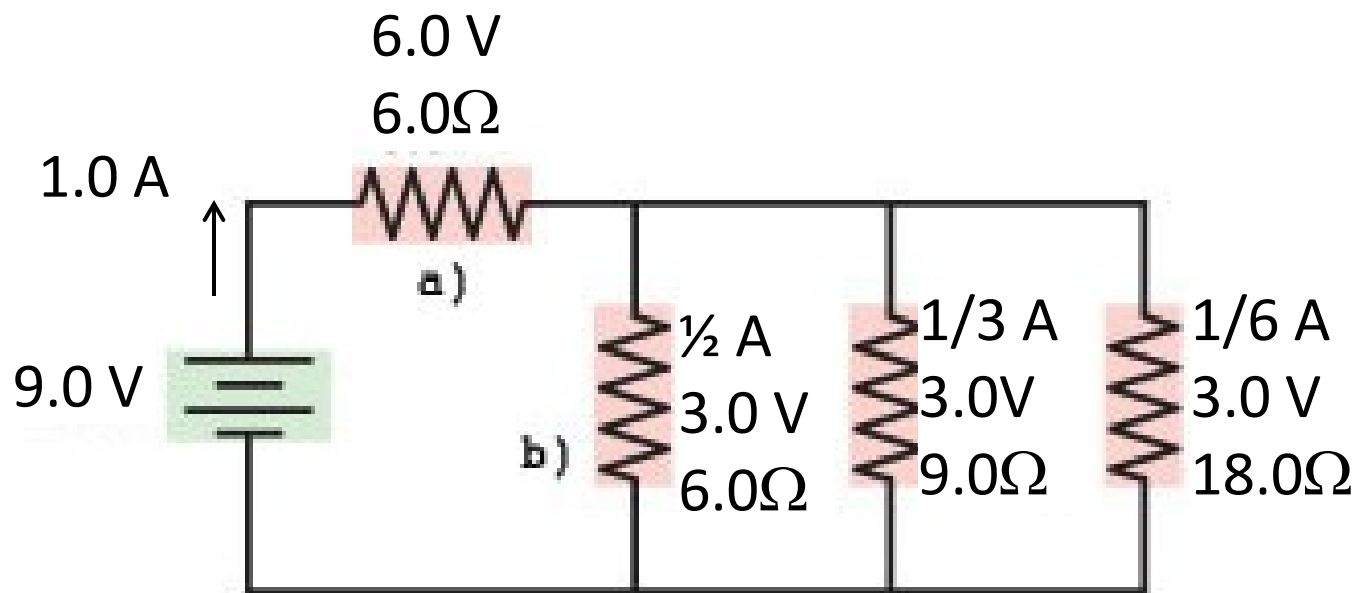

2012 Exam problem

1. The bottom of a blender has a tag that says all sorts of things and the only lines with numbers read: “Service no. 4094”, “500 Watts max”, “120 Vac 50/60Hz”.
 - A. What is the power used by this blender?
 - B. How much current does this blender draw?
 - C. What is the potential difference across the blender?
 - D. If electricity is \$0.12/ kWh, how much will it cost to run the blender for $\frac{1}{6}$ of an hour?

2012 Exam problem

1. The bottom of a blender has a tag that says all sorts of things and the only lines with numbers read: “Service no. 4094”, “500 Watts max”, “120 Vac 50/60Hz”.

A. What is the power used by this blender? **500 Watts**

B. How much current does this blender draw?

$$P = I\Delta V \text{ so } I = 500 \text{ W}/120\text{V} = \mathbf{4.17 \text{ A}}$$

A. What is the potential difference across the blender? **120 V**

B. If electricity is \$0.12/ kWh, how much will it cost to run the blender for 1/6 of an hour? $500 \text{ W} = 0.5 \text{ kW} * 1/6 \text{ hr} = 0.083\text{kWh}$ $0.083\text{kWh} * \$0.12/\text{kWh} = \mathbf{\$0.01}$