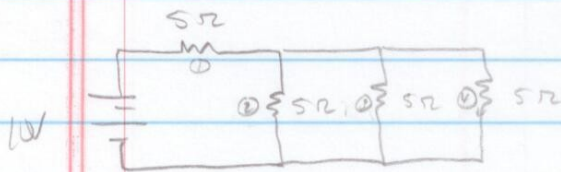



Ch 23 25, 52




Find the current through and potential difference across each resistor

- Reduce the circuit to one equivalent resistor
The 3 resistors on the right are in parallel
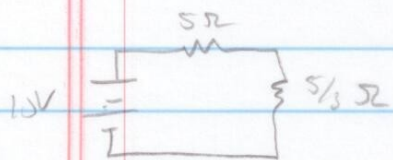
$$\frac{1}{5} + \frac{1}{5} + \frac{1}{5} = \frac{1}{R_{234}} \quad R_{234} = \frac{5}{3} \Omega$$



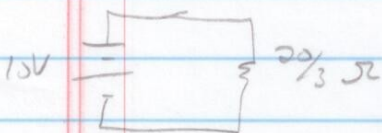
Now 5Ω and $\frac{5}{3}\Omega$ resistor are in series
 $R_{eq} = 5\Omega + \frac{5}{3}\Omega = \frac{20}{3}\Omega$



- Now you can find the total current flowing in the circuit


$$V = IR \quad \text{so} \quad I = \frac{V}{R} = \frac{10V}{6.67\Omega} = \underline{1.5A}$$

- Now build back out

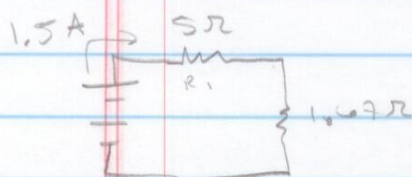

$$\Delta V_1 = I_1 R_1 = 1.5A \cdot 5\Omega = \underline{7.5V}$$
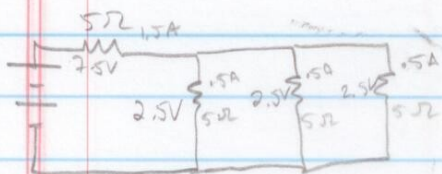
$$\Delta V_{234} = I_{234} R_{234} = 1.5A \cdot \frac{5}{3}\Omega = \underline{2.5V}$$



$\Delta V_{234} = \Delta V_2 = \Delta V_3 = \Delta V_4$ because they are in parallel

$$I_2 = \frac{V_2}{R_2} = \frac{2.5V}{5\Omega} = \underline{0.5A}$$

$$I_3 = \frac{V_3}{R_3} = \frac{2.5V}{5\Omega} = \underline{0.5A}$$


$$I_4 = \frac{V_4}{R_4} = \frac{2.5V}{5\Omega} = \underline{0.5A}$$

52. Two 75W lightbulbs are wired in series, then the combination is attached to a 120V supply. How much power is dissipated by each bulb?

A bulb that is marked 75W is assuming that it's supplied directly with 120V as it would be in a North American residence.


Find the resistance of a 75W bulb, then you can build the circuit.
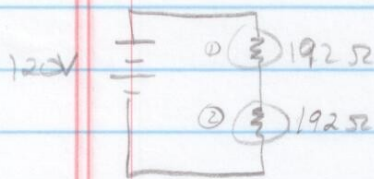
$$P = V^2/R \quad \text{so} \quad R = V^2/P = \frac{(120V)^2}{75W} = 192\Omega$$



Find current through the circuit and then use $P = I^2 R$
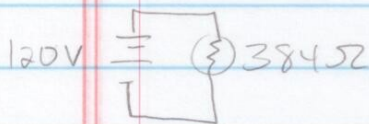
$$R_{TOT} = 192\Omega + 192\Omega = 384\Omega$$



$$I = V/R = \frac{120V}{384\Omega} = 0.3125A$$

$$P_1 = (0.3125A)^2 \cdot 192\Omega = \boxed{18.75W}$$

$$P_2 = (0.3125A)^2 \cdot 192\Omega = 18.75W$$