

Quiz #9
Physics 221

Names: Solution

1. A capacitor has an electric field of $4.0 \times 10^5 \text{ V/m}$ between the plates. If the plates have an area of $2 \times 10^{-4} \text{ m}^2$ and are separated by 5 mm, find
- The energy stored between the plates.
 - If a proton is placed 1 mm from the positive plate, what is the magnitude of the acceleration of the proton?
 - If a proton is placed 1 mm from the negative plate, what is the magnitude of the acceleration of the proton?

EMF stored in a capacitor.

$$a) U_c = \frac{1}{2} Q \Delta V = \frac{1}{2} C \Delta V^2 = \frac{1}{2} Q^2 / C$$

$$\vec{E} = 4.0 \times 10^5 \text{ V/m}$$

$$\Delta V = -E \Delta x = 4.0 \times 10^5 \text{ V/m} \cdot 5 \times 10^{-3} \text{ m} = 2000 \text{ V} \leftarrow \text{This is very large!}$$

$$C = \frac{\epsilon_0 A}{d} = \frac{8.85 \times 10^{-12} \frac{\text{C}^2}{\text{Nm}} \cdot 2 \times 10^{-4} \text{ m}^2}{5 \times 10^{-3} \text{ m}} = 3.54 \times 10^{-13} \text{ F}$$

$$U_c = \frac{1}{2} C \Delta V^2$$

$$= \frac{1}{2} 3.54 \times 10^{-13} \text{ F} \cdot (2000 \text{ V})^2$$

$$U_c = \boxed{7.08 \times 10^{-7} \text{ J}}$$


$$b) \vec{F} = q\vec{E} \quad \& \quad \vec{F} = m\vec{a} \quad \text{so} \quad q\vec{E} = m\vec{a}$$

$$\vec{a} = \frac{q\vec{E}}{m} = \frac{1.6 \times 10^{-19} \text{ C} \cdot 4.0 \times 10^5 \text{ V/m}}{1.67 \times 10^{-27} \text{ kg}} = \boxed{3.83 \times 10^{13} \text{ m/s}^2}$$

c) same as b)

The electric field of a capacitor is uniform. No matter where you place the proton between the plates, it feels the same force.

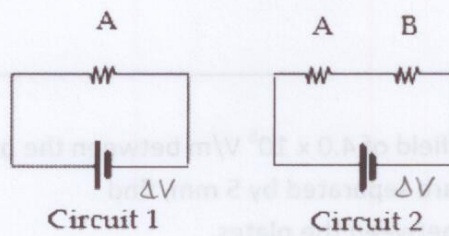2. How does the power delivered to resistor A change when resistor B is added?




$$\Delta V_A + \Delta V_B = \Delta V$$

Potential difference has to divide between A & B so A has less power than before.

- a. Power of A in circuit 1 is greater than Power of A in circuit 2
 b. Power of A in circuit 1 is less than power of A in circuit 2
 c. Power of A in circuit 1 is equal to the power of A in circuit 2

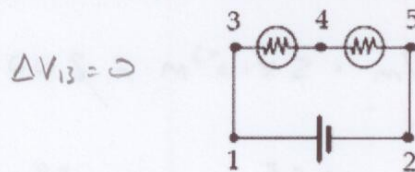3. Rank the potential difference between points 1 and 2, points 1 and 3, points 3 and 4, and points 4 and 5 in the circuit shown below from highest to lowest.



$$\Delta V_{25} = 0$$

$$\Delta V_{12} = \Delta V_{34} + \Delta V_{45}$$

- a. $\Delta V_{12} > \Delta V_{34} = \Delta V_{45} > \Delta V_{13}$
 b. $\Delta V_{12} = \Delta V_{34} = \Delta V_{45} > \Delta V_{13}$
 c. $\Delta V_{12} > \Delta V_{34} > \Delta V_{45} > \Delta V_{13}$
 d. $\Delta V_{13} > \Delta V_{34} > \Delta V_{45} > \Delta V_{13}$
 e. None of the above: _____

$$\Delta V = IR$$

$$\text{proton mass: } 1.67 \times 10^{-27} \text{ kg}$$

$$I = \Delta Q / \Delta t$$

$$P = I\Delta V = (\Delta V)^2 / R = I^2 R$$